



AP Physics C: Electricity and Magnetism 2000 Student Samples

The materials included in these files are intended for non-commercial use by AP teachers for course and exam preparation; permission for any other use must be sought from the Advanced Placement Program. Teachers may reproduce them, in whole or in part, in limited quantities, for face-to-face teaching purposes but may not mass distribute the materials, electronically or otherwise. These materials and any copies made of them may not be resold, and the copyright notices must be retained as they appear here. This permission does not apply to any third-party copyrights contained herein.

These materials were produced by Educational Testing Service (ETS), which develops and administers the examinations of the Advanced Placement Program for the College Board. The College Board and Educational Testing Service (ETS) are dedicated to the principle of equal opportunity, and their programs, services, and employment policies are guided by that principle.

The College Board is a national nonprofit membership association dedicated to preparing, inspiring, and connecting students to college and opportunity. Founded in 1900, the association is composed of more than 3,900 schools, colleges, universities, and other educational organizations. Each year, the College Board serves over three million students and their parents, 22,000 high schools, and 3,500 colleges, through major programs and services in college admission, guidance, assessment, financial aid, enrollment, and teaching and learning. Among its best-known programs are the SAT[®], the PSAT/NMSQT[™], the Advanced Placement Program[®] (AP[®]), and Pacesetter[®]. The College Board is committed to the principles of equity and excellence, and that commitment is embodied in all of its programs, services, activities, and concerns.

Copyright © 2001 by College Entrance Examination Board. All rights reserved. College Board, Advanced Placement Program, AP, and the acorn logo are registered trademarks of the College Entrance Examination Board.


PHYSICS C

Section II, ELECTRICITY AND MAGNETISM

Time—45 minutes

3 Questions

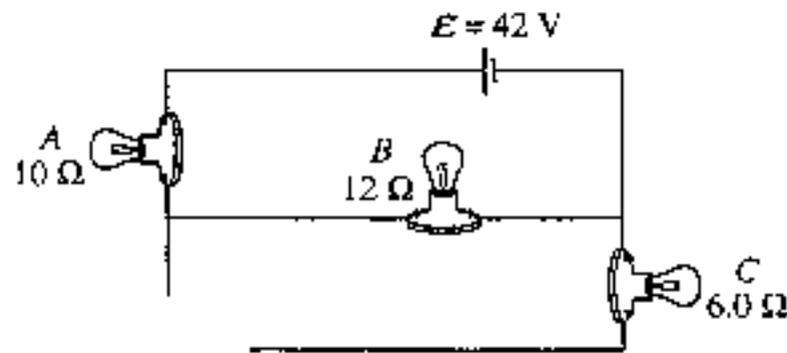
Directions: Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in this booklet in the spaces provided after each part, NOT in the green insert.



E & M 1.

Lightbulbs *A*, *B*, and *C* are connected in the circuit shown above.

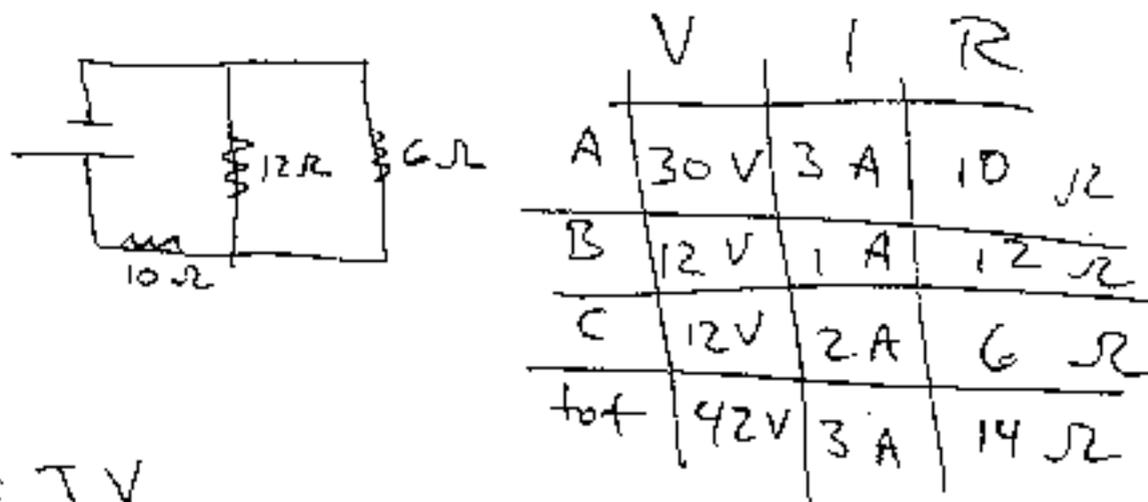- (a) List the bulbs in order of their brightness, from brightest to least bright. If any bulbs have the same brightness, state which ones. Justify your answer.



$P = IV$

$P_A = 3(30) = 90 \text{ W}$

$P_B = 1(12) = 12 \text{ W}$

$P_C = 2(12) = 24 \text{ W}$

Brightest = A
 Next = C
 Least = B

GO ON TO THE NEXT PAGE.


PHYSICS C

Section II, ELECTRICITY AND MAGNETISM

Time—45 minutes

3 Questions

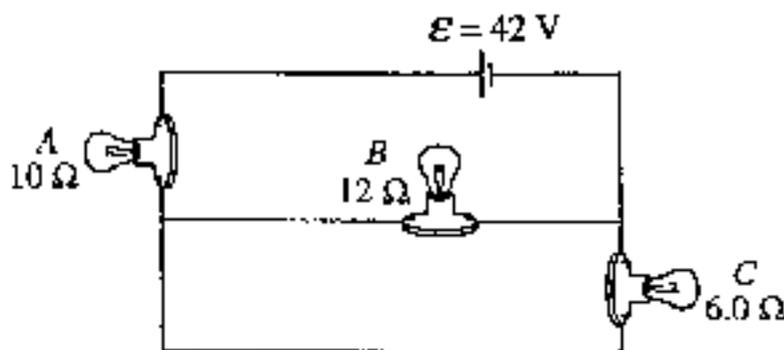Directions: Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in this booklet in the spaces provided after each part, NOT in the green insert.



E & M 1.

Lightbulbs A , B , and C are connected in the circuit shown above.


- (a) List the bulbs in order of their brightness, from brightest to least bright. If any bulbs have the same brightness, state which ones. Justify your answer.

$$P = I^2 R$$

Lightbulb A has the brightest light, because all current must run through it so it has the greatest I , and \therefore the most power

Lightbulb C is the second brightest since it has less resistance than Lightbulb B , which means more current and \therefore more power according to $P = I^2 R$

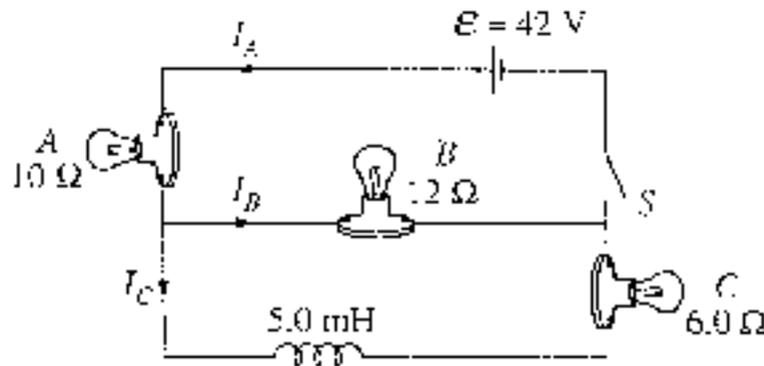
Lightbulb B has the least brightness, because it has the least current pass through it.



Now a switch S and a 5.0 mH inductor are added to the circuit, as shown above. The switch is closed at time $t = 0$.

(b) Determine the currents I_A , I_B and I_C for the following times.

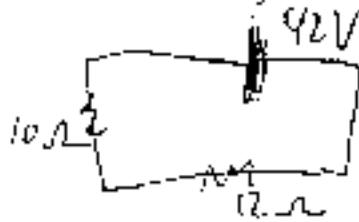i. Immediately after the switch is closed



$$V = I R$$

$$42 \text{ V} = I_A (22 \Omega)$$

$$I_A = 1.9 \text{ A}$$

$$V = I_B R$$

$$42 \text{ V} = I_B (22 \Omega)$$

$$I_B = 1.9 \text{ A}$$

$$I_C = I_{\text{max}} (1 - e^{-t/\tau})$$

$$I_C = 0 \text{ A}$$

ii. A long time after the switch is closed



$$V = I_A R$$

$$42 \text{ V} = I_A (14 \Omega)$$

$$I_A = 3 \text{ A}$$

$$R_T = 10 \Omega + \left(\frac{1}{12} + \frac{1}{6} \right)^{-1} = 14 \Omega$$

$$I_B = 3 \text{ A} \left(\frac{6}{12+6} \right)$$


$$I_B = 3 \left(\frac{6}{18} \right)$$

$$I_B = 1 \text{ A}$$

$$3 \text{ A} - 1 \text{ A} = I_C$$

$$I_C = 2 \text{ A}$$

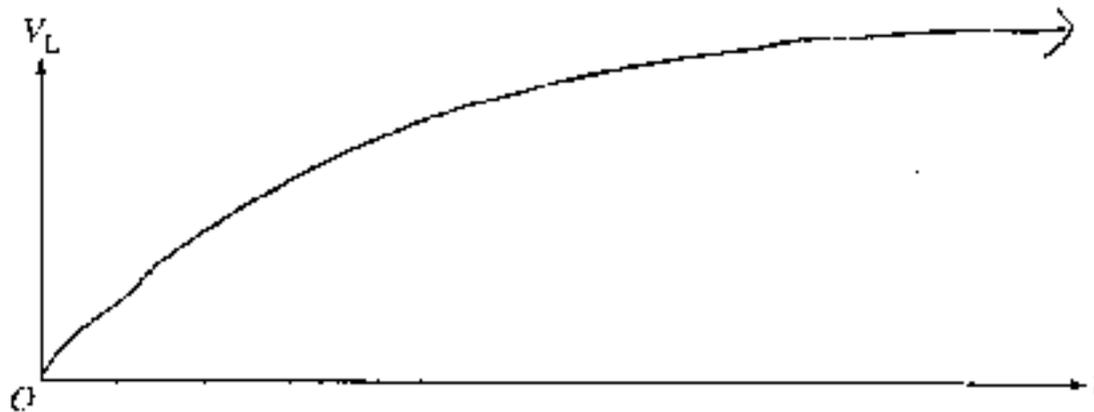(c) On the axes below, sketch the magnitude of the potential difference V_L across the inductor as a function of time, from immediately after the switch is closed until a long time after the switch is closed.




PHYSICS C

Section II, ELECTRICITY AND MAGNETISM

Time—45 minutes

3 Questions

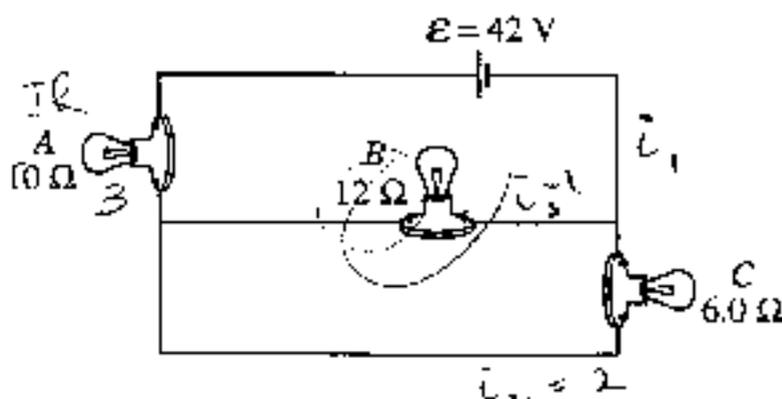Directions: Answer all three questions. The suggested time is about 15 minutes for answering each of the questions, which are worth 15 points each. The parts within a question may not have equal weight. Show all your work in this booklet in the spaces provided after each part, NOT in the green insert.



E & M 1.

Lightbulbs A, B, and C are connected in the circuit shown above.

- (a) List the bulbs in order of their brightness, from brightest to least bright. If any bulbs have the same brightness, state which ones. Justify your answer.

$$\frac{1}{R_{AC}} = \frac{1}{12\Omega} + \frac{1}{6\Omega}$$

$$R_{AC} = 4\Omega$$

$$R_{AC} < R_A, R_C < R_B$$

Therefore:

Brightest

A

$$i = \frac{42}{10+4} = 3 \text{ amp}$$

C

$$i = \frac{12}{6} = 2 \text{ amp}$$

Least bright

B

$$i = \frac{12}{12} = 1 \text{ amp}$$

$$\epsilon - 10i - 4i = 0$$

$$42 = 14i$$


$$i = 3 \text{ amp}$$

$$V_{BC} = 42 - 10(3) = 12 \text{ V}$$

since $V = IR$,
and V is constant between
B and C, Lower R means

Lower I and
Lower brightness.

A has higher R ,
but also higher V

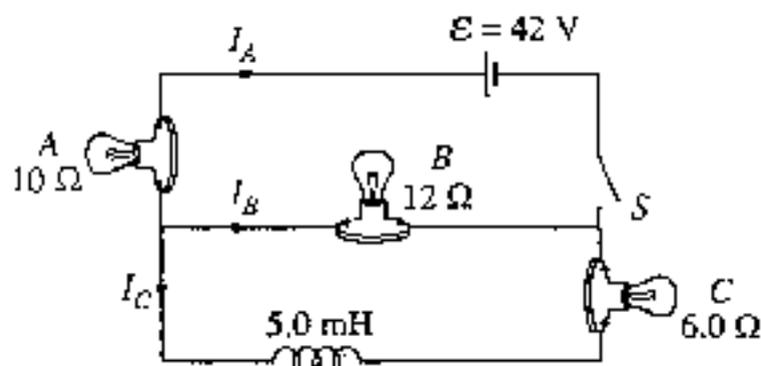

Now a switch S and a 5.0 mH inductor are added to the circuit, as shown above. The switch is closed at time $t = 0$.


(b) Determine the currents I_A , I_B , and I_C for the following times.

i. Immediately after the switch is closed

$$I_A = I_B = \frac{V}{R} = \frac{42}{10+12} = 1.9 \text{ amp}$$


ii. A long time after the switch is closed

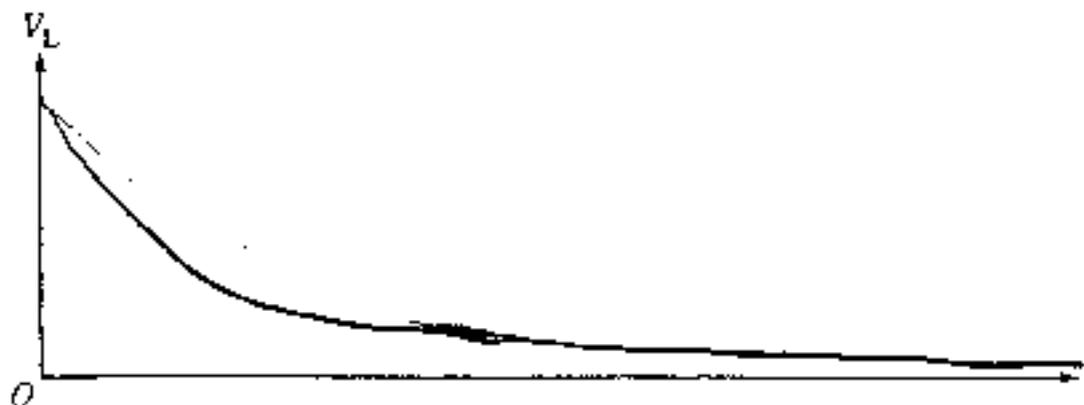(c) On the axes below, sketch the magnitude of the potential difference V_L across the inductor as a function of time, from immediately after the switch is closed until a long time after the switch is closed.



$$\mathcal{E} = -L \frac{dI}{dt}$$

GO ON TO THE NEXT PAGE.

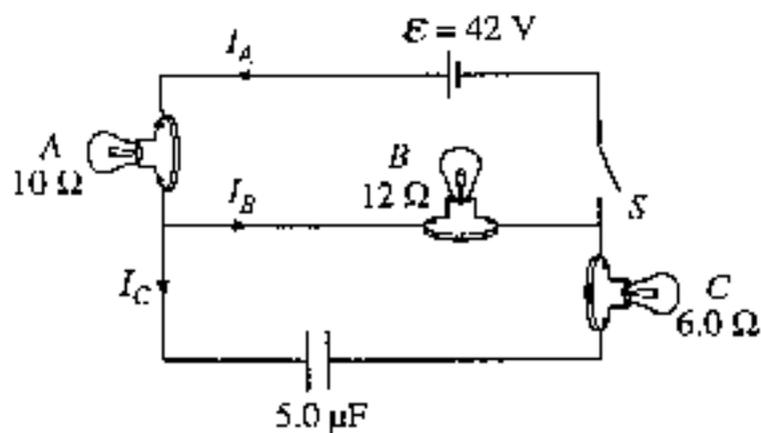

- (d) Now consider a similar circuit with an uncharged 5.0 μF capacitor instead of the inductor, as shown above. The switch is again closed at time $t = 0$. On the axes below, sketch the magnitude of the potential difference V_{cap} across the capacitor as a function of time, from immediately after the switch is closed until a long time after the switch is closed.

