




AP[®] Physics C: Electricity and Magnetism 2001 Sample Student Responses

The materials included in these files are intended for non-commercial use by AP teachers for course and exam preparation; permission for any other use must be sought from the Advanced Placement Program. Teachers may reproduce them, in whole or in part, in limited quantities, for face-to-face teaching purposes but may not mass distribute the materials, electronically or otherwise. These materials and any copies made of them may not be resold, and the copyright notices must be retained as they appear here. This permission does not apply to any third-party copyrights contained herein.

These materials were produced by Educational Testing Service (ETS), which develops and administers the examinations of the Advanced Placement Program for the College Board. The College Board and Educational Testing Service (ETS) are dedicated to the principle of equal opportunity, and their programs, services, and employment policies are guided by that principle.

The College Board is a national nonprofit membership association dedicated to preparing, inspiring, and connecting students to college and opportunity. Founded in 1900, the association is composed of more than 3,900 schools, colleges, universities, and other educational organizations. Each year, the College Board serves over three million students and their parents, 22,000 high schools, and 3,500 colleges, through major programs and services in college admission, guidance, assessment, financial aid, enrollment, and teaching and learning. Among its best-known programs are the SAT[®], the PSAT/NMSQT[™], the Advanced Placement Program[®] (AP[®]), and Pacesetter[®]. The College Board is committed to the principles of equity and excellence, and that commitment is embodied in all of its programs, services, activities, and concerns.

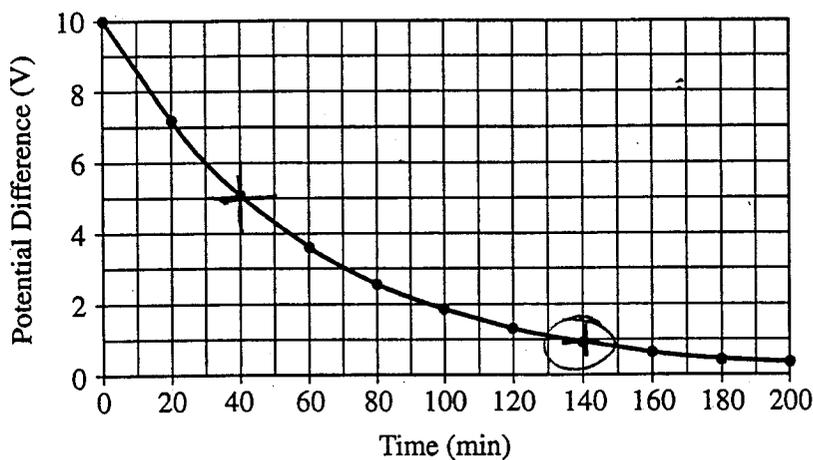Copyright © 2001 by College Entrance Examination Board. All rights reserved. College Board, Advanced Placement Program, AP, and the acorn logo are registered trademarks of the College Entrance Examination Board.



E & M 2.

You have been hired to determine the internal resistance of $8.0 \mu\text{F}$ capacitors for an electronic component manufacturer. (Ideal capacitors have an infinite internal resistance—that is, the material between their plates is a perfect insulator. In practice, however, the material has a very small, but nonzero, conductivity.) You cannot simply connect the capacitors to an ohmmeter, because their resistance is too large for an ohmmeter to measure. Therefore you charge the capacitor to a potential difference of 10 V with a battery, disconnect it from the battery and measure the potential difference across the capacitor every 20 minutes with an ideal voltmeter, obtaining the graph shown above.

(a) Determine the internal resistance of the capacitor.

$$V = V_0 e^{-t/\tau} \quad \tau = RC = R \cdot 8 \times 10^{-6} \quad 140 \text{ min} \cdot 60 \frac{\text{sec}}{\text{min}} = 8400 \text{ s}$$

$$V = 10 \cdot e^{-8400/\tau}$$

$$\ln \frac{1}{10} = -8400/\tau$$

$$3600 = R \cdot 8 \times 10^{-6}$$

$$\tau = 3600 \text{ s}$$

$$R = 4.5 \times 10^8 \Omega$$

The capacitor can be approximated as a parallel-plate capacitor separated by a 0.10 mm thick dielectric with $\kappa = 5.6$.

(b) Determine the approximate surface area of one of the capacitor "plates."

$$C = \kappa \frac{\epsilon_0 A}{s}$$

$$8 \times 10^{-6} = \frac{8.85 \times 10^{-12} \cdot A}{.0001} \cdot 5.6$$

$$A = 16.1 \text{ m}^2$$

GO ON TO THE NEXT PAGE.

(c) Determine the resistivity of the dielectric.

$$R = \rho \frac{l}{A} \quad 4.5 \times 10^8 = \rho \cdot \frac{.0001}{16.1}$$

$$\rho = 7.25 \times 10^{13} \Omega \cdot m$$

(d) Determine the magnitude of the charge leaving the positive plate of the capacitor in the first 100 min.

$$V = IR \quad I = \frac{V}{R} = \frac{V_0 e^{-t/\tau}}{R}$$

$$Q = \int_0^b I dt$$

$$Q = \int_0^{6000} \frac{10 \cdot e^{-t/3600}}{4.5 \times 10^8} dt = 2.2 \times 10^{-8} \int_0^{6000} e^{-t/3600} dt =$$

$$6.5 \times 10^{-5} C$$

EEEEEEEEEEEEEEEEEEEE

(c) Determine the resistivity of the dielectric.

$$R = \frac{\rho l}{A}$$

$$\rho = \frac{RA}{l}$$

$$= \frac{(4.5 \times 10^8 \Omega)(16.14 \text{ m})}{(1 \times 10^{-3})}$$

$$\rho = 7.26 \times 10^{13}$$

(d) Determine the magnitude of the charge leaving the positive plate of the capacitor in the first 100 min.

$$\textcircled{a} \quad t = 0 \quad V = 10, \quad C = 8 \times 10^{-6}$$
$$Q = 8 \times 10^{-5}$$

$$\textcircled{b} \quad t = 100 \quad V = 2, \quad C = 8 \times 10^{-6}$$
$$Q = 1.6 \times 10^{-5}$$

$$\Delta Q = 6.4 \times 10^{-5} \text{ C}$$

GO ON TO THE NEXT PAGE.